

University of Illinois at Urbana-Champaign  
Dept. of Electrical and Computer Engineering

## ECE 120: Introduction to Computing

### Bit-Sliced Comparator

## How Do You Compare Unsigned Numbers?

Let's develop a bit-sliced design to  
**compare two unsigned numbers.**

**Which 8-bit unsigned number is bigger?**

```
0 1 1 0 1 0 0 0
0 1 0 1 0 1 1 1
```

How did you know?  
Did you start on the left or the right?

## Humans Go from Left to Right

Usually, humans start on the left. Why?  
As soon as we notice a difference, we're done!

humans compare this way

```

0 1 1 a4a3a2a1a0
0 1 0 b4b3b2b1b0

```

Bit-sliced hardware cannot stop in the middle.  
The information flows from one end to the other.  
Output wires produce the answer (in bits).

## Our Design Compares from Right to Left

Our comparator design will start on the right.

humans compare this way

```

a7a6a5a4a3a2a1a0
b7b6b5b4b3b2b1b0

```

our design will compare this way

From least significant to most significant bit.

## Three Possible Answers for Comparison of A and B

When comparing two numbers, **A** and **B**, we have **three possible outcomes**:

$$A < B$$

$$A = B$$

$$A > B$$

To decide the answer for **N+1** bits, we need:

- the answer for **N** (less significant) bits,
- one bit of **A**, and
- one bit of **B**.


## An Abstract Model of the Comparator Bit Slice

A question for you:

**How many bits must pass between slices?**

 **Two!**

This figure shows an abstract model of our bit slice.



## We Need a Representation for Answers

Another question for you:

**How do we represent the three possible answers?**

**Any way we want!**

Our choice of representation will affect the amount of logic we need.

Here's a good one...

$C_1$	$C_0$	meaning
0	0	<b>A = B</b>
0	1	<b>A &lt; B</b>
1	0	<b>A &gt; B</b>
1	1	not used

## A Single Bit Requires Two Minterms on A, B

Let's start by solving a single bit.

In this case, there are no less significant bits.

So we consider only **A** and **B**.

Fill in the meanings, then the bits.


Note that **Z<sub>1</sub>** and **Z<sub>0</sub>** are minterms.

<b>A</b>	<b>B</b>	<b>Z<sub>1</sub></b>	<b>Z<sub>0</sub></b>	meaning
0	0	0	0	<b>A = B</b>
0	1	0	1	<b>A &lt; B</b>
1	0	1	0	<b>A &gt; B</b>
1	1	0	0	<b>A = B</b>
 
## Comparing Two Bits is Fairly Easy

An implementation for a single bit appears below.

This structure forms the core of our bit slice, since it compares one bit of **A** with one bit of **B**.



## When A and B are Equal, Pass Along the Answer

Now for the full problem.

We'll start with the case of **A = 0** and **B = 0**.

A	B	C <sub>1</sub>	C <sub>0</sub>	meaning	Z <sub>1</sub>	Z <sub>0</sub>	meaning
0	0	0	0	<b>A = B</b>	0	0	<b>A = B</b>
0	0	0	1	<b>A &lt; B</b>	0	1	<b>A &lt; B</b>
0	0	1	0	<b>A &gt; B</b>	1	0	<b>A &gt; B</b>
0	0	1	1	???	<b>x</b>	<b>x</b>	don't care

## When A and B are Equal, Pass Along the Answer

Is there any difference when **A = 1** and **B = 1**?

**No, outputs are the same as the last case.**

A	B	C <sub>1</sub>	C <sub>0</sub>	meaning	Z <sub>1</sub>	Z <sub>0</sub>	meaning
1	1	0	0	<b>A = B</b>	0	0	<b>A = B</b>
1	1	0	1	<b>A &lt; B</b>	0	1	<b>A &lt; B</b>
1	1	1	0	<b>A &gt; B</b>	1	0	<b>A &gt; B</b>
1	1	1	1	???	<b>x</b>	<b>x</b>	don't care

## When A and B Differ, Override the Previous Answer

What about case of **A = 0** and **B = 1**?

**Always output A < B (for valid inputs).**

A	B	C <sub>1</sub>	C <sub>0</sub>	meaning	Z <sub>1</sub>	Z <sub>0</sub>	meaning
0	1	0	0	<b>A = B</b>	0	1	<b>A &lt; B</b>
0	1	0	1	<b>A &lt; B</b>	0	1	<b>A &lt; B</b>
0	1	1	0	<b>A &gt; B</b>	0	1	<b>A &lt; B</b>
0	1	1	1	???	<b>x</b>	<b>x</b>	don't care

## When A and B Differ, Override the Previous Answer

And the case of  $A = 1$  and  $B = 0$ ?

Always output  $A > B$  (for valid inputs).

A	B	$C_1$	$C_0$	Meaning	$Z_1$	$Z_0$	meaning
1	0	0	0	$A = B$	1	0	$A > B$
1	0	0	1	$A < B$	1	0	$A > B$
1	0	1	0	$A > B$	1	0	$A > B$
1	0	1	1	???	x	x	don't care

## $Z_1$ is a Majority Function

Let's use a K-map to solve  $Z_1$ .

What are the loops?

$AB'$

$AC_1$

$B'C_1$

So

$$Z_1 = AB' + AC_1 + B'C_1$$

		AB			
		00	01	11	10
$C_1C_0$	00	0	0	0	1
	01	0	0	0	1
	11	x	x	x	x
	10	1	0	1	1

## $Z_0$ is Also a Majority Function

Now let's use a K-map to solve  $Z_0$ .

What are the loops?

$A'B$

$A'C_0$

$BC_0$

So

$$Z_0 = A'B + A'C_0 + BC_0$$

		AB			
		00	01	11	10
$C_1C_0$	00	0	1	0	0
	01	1	1	1	0
	11	x	x	x	x
	10	0	1	0	0

## Full Implementation as SOP Expressions

$$Z_1 = AB' + AC_1 + B'C_1$$

$$Z_0 = A'B + A'C_0 + BC_0$$

Notice the symmetry.

And the single-bit core.

